

Keywords: PWM, DAC, ADC, PIC, microcontroller, uc, MCU, low power, analog digital converter, digital analog converters, a/d d/a converter

APPLICATION NOTE 1031

Low-Power 3V ADC is 0.05% Linear

Jul 09, 1998

Abstract: This application note describes using a microcontroller (μ C) with integrated digital-to-analog converter (DAC) and comparators to create a low cost ADC that is 0.05% linear.

The simple 3V analog-to-digital converter (ADC) shown in **Figure 1** is very small, requires no negative supply or expensive precision components, and draws minimal supply current (10 μ A). A single conversion consists of 12,000 comparisons and takes about 300ms. The circuit operates as described below.

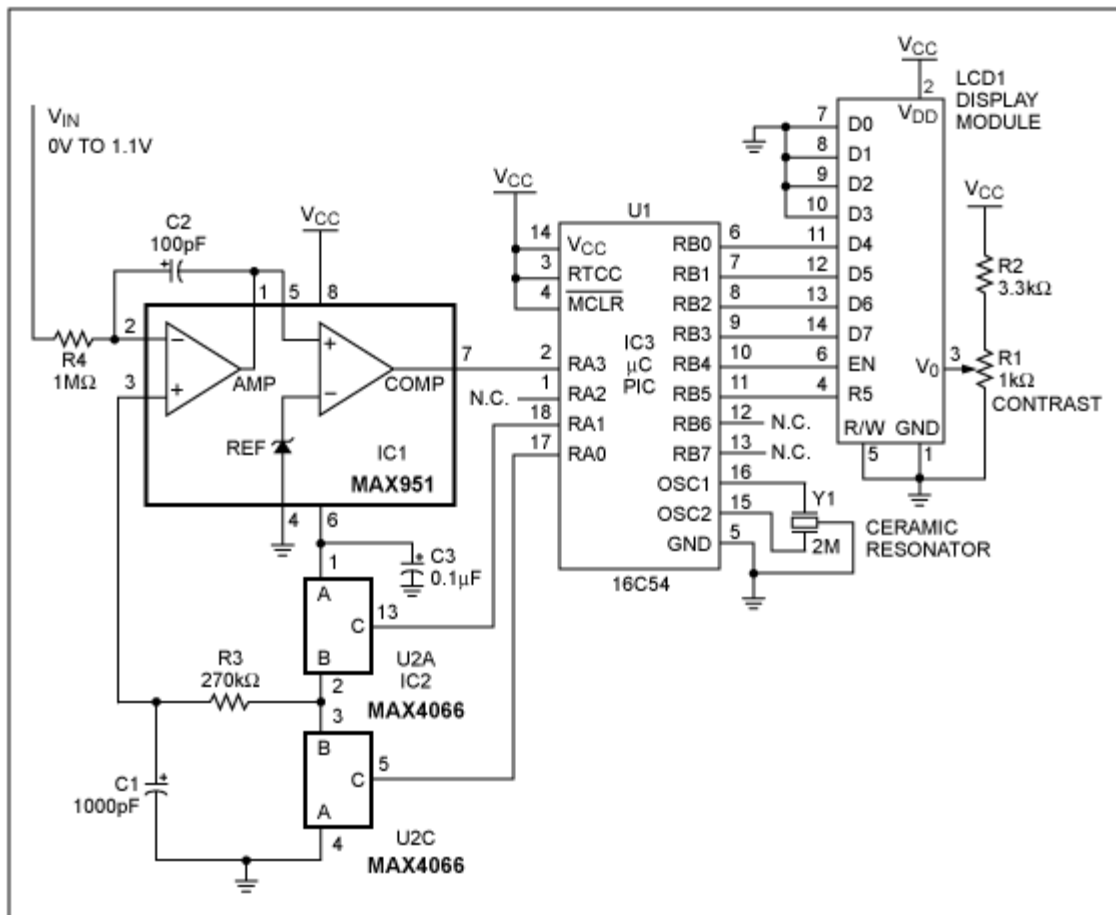


Figure 1. This inexpensive, 0.05%-linear ADC can be added to existing equipment or used to upgrade the converter included in certain μ Cs (such as the PIC 16C71).

Following each comparison, the microcontroller (μ C) closes one of two switches: IC2A (comparator high) or IC2B (comparator low). The switches connect either V_{REF} (1.2V) or ground to their "B" terminals, producing a pulse-width modulation (PWM) signal that is filtered by R3 and C1 and differentially integrated against V_{IN} . The result is compared against V_{REF} .

As this action integrates the error voltage up and down, the μ C counts the number of comparisons for which the comparator output is high (IC2A switch closed). This count (N_H) divided by 12,000 equals the PWM duty cycle. The system is fully ratiometric, so the duty cycle equals $N_H/12000 = V_{IN}/V_{REF}$. Rearranging and substituting $V_{REF} = 1.2V$ yields $V_{IN} = N_H/10,000$.

Listing 1* enables the the LCD module to display voltage values directly, like a digital panel meter. The subroutine "DVM" produces the actual A/D-conversion values required in an embedded application. Setting the span constant (number of comparisons) to 12,000 yields a 300ms conversion with 4-1/2 digits of resolution and produces a 1.1999 full-scale display. You can speed the conversion to 30ms by setting the span constant to 1200, which produces a 3-1/2 digit display that reads 1.199 at full scale.

IC2's near-ideal switching characteristics account for the low 0.05% nonlinearity. A high-performance, 3V-specified version of the industry standard 4066, IC2 is a quad analog switch that features 35 Ω on-resistances and 0.1nA (max) off leakages. You can save space by replacing IC2 with the MAX323 dual analog switch: a 3V single-pole/single-throw device with specifications similar to those of the MAX4066. The MAX323 resides in an 8-pin μ MAX package (versus a 14-pin SO for the MAX4066).

V_{CC} is limited to the maximum allowed by the μ C (6V). IC1, which operates with V_{CC} as low as 2.8V over temperature, draws only 7 μ A of supply current. The voltage reference in IC1 is stable for capacitive loads smaller than 100pF or larger than 0.05 μ F. To ensure stability, the reference's external bypass capacitor (C3) should be kept large.

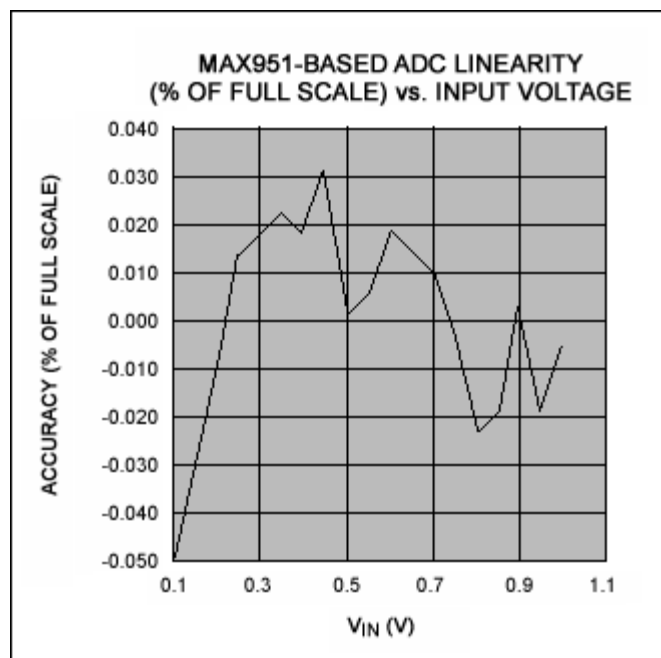


Figure 2. In Figure 1, the output nonlinearity (as a percentage of full scale) varies as shown.

A similar version of this article appeared in the June 19, 1997 issue of *EDN* magazine.

Related Parts

MAX4066	Low-Cost, Low-Voltage, Quad, SPST, CMOS Analog Switch	Free Samples
MAX951	Ultra-Low-Power, Single-Supply Op Amp + Comparator + Reference	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 1031: <http://www.maximintegrated.com/an1031>

APPLICATION NOTE 1031, AN1031, AN 1031, APP1031, Appnote1031, Appnote 1031

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>